

数字逻辑

Chap 1 Digital Systems and Information

1.1 signal - Binary values

Analog (模拟信号) continuous: value & time

Time sequence signal:

用物理属性代表二进制制例证: (见右侧列表)

CPU - Voltage

Disk - Magnetic Field Direction

CD - Surface Pits/Light

Dynamic RAM - Electrical Charge

Uses for the XOR: 1. The controllable source/inverted output

$$A \oplus 0 = A \quad A \oplus 1 = \bar{A}$$

2. Digital comparator

3. half adder

$$A \oplus A = 0 \quad A \oplus \bar{A} = 1 \quad \text{Truth table without carry}$$

NOR: 

$$F \oplus F = T$$

$$T \oplus F = F$$

$$F \oplus T = F$$

$$T \oplus T = T$$

2.3 Logic Functions Simplification

2.3.1 An application of Boolean algebra

Contain the smallest number of literals

The most simple expression is not unique

① AND-OR style

"AND-item" 尽可能少, 前提是每个 item 的变量越少越好

$$F = A + CD$$

and item

② OR-AND style

"OR-item" 尽可能少

OR-AND $\xleftrightarrow{\text{duality}}$ AND-OR

2.4 Standard forms / Canonical Forms (范式)

① Sum of Minterms (SOM) ② Product of Maxterms (POM)

Minterms (最小项): 所有变量都以原变量或反变量形式出现 (仅出现一次)

例: 对于 X, Y: XY, X \bar{Y} , $\bar{X}Y$, $\bar{X}\bar{Y}$ 为最小项 对 n 个变量有 2ⁿ 个最小项

性质: (1) 所有最小项同时只有一个值为 1 (2) 两最小项之和为 0 $m_i \cdot m_j = 0$

(3) 所有最小项之和 $\sum m_i = 1$ (4) 任何不在 F 中的最小项均可反函数 \bar{F}

Maxterms (最大项): 所有变量都以原变量或反变量形式出现 (仅出现一次)

性质: (1) 所有最大项同时只有一个值为 1 (2) 两最大项之和为 1 $M_i + M_j = 1$

(3) 所有最大项之积 $\prod M_i = 0$

两者关系: (1) M_i 与 m_j 互反 $M_3 = \bar{A}BC \quad M_3 = A + \bar{B} + \bar{C}$

(2) $\sum m_i$ and $\prod M_i$ is each other Duality $m_3 = \bar{M}_3$

(3) $F = \sum m_i = \prod \bar{M}_i$ 记号 $F_{min}(X, Y, Z) = m_0 + m_2 + m_5 + m_7 = \sum(0, 2, 5, 7)$

$F_{max}(X, Y, Z) = M_1 \cdot M_3 \cdot M_4 \cdot M_6 = \prod(1, 3, 4, 6)$

SOP: $ABC + \bar{A}BC + B$ Pos: $(A+B)(A+\bar{B}+\bar{C})$

This form often can be simplified (so corresponding circuit is simpler)

2.5 Karnaugh map of Function (卡诺图函数)

每一格代表一个最小项

n=2

n=3

n=4

排列成类似格雷码

1-dimensional block can eliminate one variable, and N-dimensional elimination N-variables

画 K-map 时尤其注意从右到左 3 列

注意一下, 容易错

画圈时注意 4 角

画圈也可以圈 0, 这样得到的是 \bar{F}

取反即可

① 写出函数最小项形式

② 画出 K-map

③ 画圈, 尽可能多圈最小项

不要遗漏, 尽可能避免重叠

④ 化简

Incompletely Specified Function


Don't care term: input

(1) not appear in the combination

(2) for some combination of inputs, there is an uncertain output

K-map 上有些格为 X, 可解释为 1 也可解释为 0

1.2 Digital System

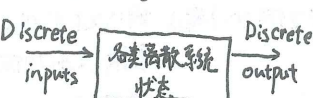

Type: ① Combination Logic system

(1) No state represent 附: multivariate

(2) $f_{output} = Func(Input)$ multi-output $F(x)$

② Sequential System

(1) state present; state update at discrete times Synchronous

(2) $f_{state} = Func(State, Input)$ any time Asynchronous

$f_{output} = Func(State) \text{ or } Func(State, Input)$

1.3 Computer Architecture

① memory ② Datapath (BUS)

③ control unit ④ CPU ⑤ I/O device

1.4 进制相关计算:

① BCD adder (当每个 BCD 和超过 9 时, 进位 BCD 进位)

$$\begin{array}{r} 448 + 489 = (0100 \ 0100 \ 1000)_{BCD} \\ + (0100 \ 1000 \ 1001)_{BCD} \\ \hline 1000 \ 1101 \ 0001 \\ + \quad \quad 0110 \ 0110 \\ \hline 1001 \ 0011 \ 0111 = 937 \end{array}$$

1.5 coding

Given n digits in radix r, there are rⁿ

distinct elements that can be represented

凡大有用编码: (不在表中的还加 Unicode & ASCII)

Decimal	8421	Excess 3	8, 4, 2, 1	Gray
0	0000	0011	0000	0000
1	0001	0100	0111	0100
2	0010	0101	0110	0101
3	0011	0110	0101	0111
4	0100	0111	0100	0110
5	0101	0100	1011	0010
6	0110	1001	1010	0011
7	0111	1010	1001	0001
8	1000	1011	1000	1001
9	1001	1100	1111	1000

② 二、八、十、十六进制相互转化

$$\begin{array}{l} 2 \rightarrow 10 \quad \text{权重开+进制相加} \\ (110 \ 0101 \ 101)_2 = 2^6 + 2^5 + 2^3 + 2^2 + 2^1 + 2^0 \\ = (813.625)_{10} \end{array}$$


10 \rightarrow 2 整数除 2 取余, 小数乘 2 取整

$$\begin{array}{l} \text{例: } (725.678)_{10} \rightarrow (725)_{10} \\ \begin{array}{r} 725 \div 2 = 362 \text{ 余 } 1 \\ 362 \div 2 = 181 \text{ 余 } 0 \\ 181 \div 2 = 90 \text{ 余 } 1 \\ 90 \div 2 = 45 \text{ 余 } 0 \\ 45 \div 2 = 22 \text{ 余 } 1 \\ 22 \div 2 = 11 \text{ 余 } 0 \\ 11 \div 2 = 5 \text{ 余 } 1 \\ 5 \div 2 = 2 \text{ 余 } 1 \\ 2 \div 2 = 1 \text{ 余 } 0 \\ 1 \div 2 = 0 \text{ 余 } 1 \end{array} \end{array}$$

偶校验 补 1 bit 使全 bit 中 1 的个数为偶数, 则补 0

xy	m ₀	m ₁	m ₂	m ₃	M ₀	M ₁	M ₂	M ₃
00	1	0	0	0	0	1	1	1
01	0	1	0	0	1	0	1	1
10	0	0	1	0	1	1	0	1
11	0	0	0	1	1	1	1	0

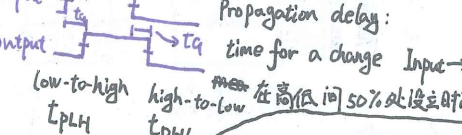Gate Delay: the output change doesn't occur instantaneously, the delay is denoted by t_g



Propagation delay: time for a change in the output to occur after a change in the input. In the high-to-low 50%处设定时点, 迟滞

No Delay

Transport Delay (TD)

Inertial Delay (ID)

Rejection time

Complementing function (反函数): \bar{F}

$$\text{例: } F = \bar{A}B + C\bar{D} \Rightarrow \bar{F} = (A + \bar{B})(\bar{C} + D)$$

Duality rules (对偶规则): AND, OR swap

0, 1 swap

Variable unchanged

Shannon formula

$$x f(x, \bar{x}, y, \dots, z_n) = x f(1, 0, y, \dots, z_n)$$

$$\bar{x} f(x, \bar{x}, y, \dots, z_n) = \bar{x} f(0, 1, y, \dots, z_n)$$

$$x + \bar{x} f(x, \bar{x}, y, \dots, z_n) = x + f(0, 1, y, \dots, z_n)$$

$$\bar{x} + f(x, \bar{x}, y, \dots, z_n) = \bar{x} + f(1, 0, y, \dots, z_n)$$

Chap 2 Boolean algebra

2.1 Binary Logic and Gates

And: $Z = X \cdot Y = XY = X \wedge Y \quad \bar{Y} = \neg Y$

Or: $Z = X + Y = X \vee Y \quad \bar{Y} = \neg Y$

Not: $Z = \bar{X} \quad x \rightarrow \neg x$

Transport delay: 输出在经过一个固定特定时间后响应输入的改变

Inertial delay: 与 transport delay 相同

除了 input 两次变化时间, 于 rejection time 的情况 (此时将不变)

Truth table 独一无二但 expression 与 logic diagrams 则非如此

2.2 Basic concepts of Boolean algebra

$$F = f(X_1, X_2, \dots, X_n)$$

Single output

multi-output

基本等式:

$$\overline{\bar{x}y} = \bar{x} \cdot \bar{y} \quad \overline{x \cdot y} = \bar{x} + \bar{y}$$

$$A(A+B) = A \quad A+\bar{A}B = A$$

$$A(\bar{A}+B) = \bar{A}B \quad A+\bar{A}B = A+B$$

$$(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$$

$$AB+\bar{A}C+BC = AB+\bar{A}C$$

$$F_1 = F_2 \Leftrightarrow \text{Truth table is completely identical}$$

Shannon expansion

$$F(x, \bar{x}, y, \dots, z_n) = x f(1, 0, y, \dots, z_n)$$

$$\bar{x} f(x, \bar{x}, y, \dots, z_n) = \bar{x} f(0, 1, y, \dots, z_n)$$

$$x + \bar{x} f(x, \bar{x}, y, \dots, z_n) = x + f(0, 1, y, \dots, z_n)$$

$$\bar{x} + f(x, \bar{x}, y, \dots, z_n) = \bar{x} + f(1, 0, y, \dots, z_n)$$

$$= [x + f(0, 1, y, \dots, z_n)] [\bar{x} + f(1, 0, y, \dots, z_n)]$$

$$= [x + f(0, 1, y, \dots, z_n)] [\bar{x} + f(1, 0, y, \dots, z_n)]$$

$$= [x + f(0, 1, y, \dots, z_n)] [\bar{x} + f(1, 0, y, \dots, z_n)]$$

$$= [x + f(0, 1, y, \dots, z_n)] [\bar{x} + f(1, 0, y, \dots, z_n)]$$